

## Problem 1

The majority function produces a false value when  $\frac{n}{2}$  of the provided inputs are false (where  $n$  is the number of inputs). This function can be trivially implemented using three AND gates and two OR gates.

$a$	$b$	$c$	$sum$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		$bc$			
		00	01	11	10
$a$	0	0	0	1	0
	1	0	1	1	1

---

```

module Majority(
    input wire a,
    input wire b,
    input wire c,
    output wire sum
);

    // Compute the products
    and(a_and_b, a, b);
    and(a_and_c, a, c);
    and(b_and_c, b, c);

    // Cascade the OR
    or(buffer, a_and_b, a_and_c);
    or(sum, buffer, b_and_c);

endmodule // Majority

```


```
module MajorityTest;

    reg a;
    reg b;
    reg c;
    wire sum;

    Majority majority(a, b, c, sum);

    initial begin
        $monitor("a = %d, b = %d, c = %d, sum = %d", a, b, c, sum);
        a = 0; b = 0; c = 0;
        #20; a = 0; b = 0; c = 1;
        #20; a = 0; b = 1; c = 0;
        #20; a = 0; b = 1; c = 1;
        #20; a = 1; b = 0; c = 0;
        #20; a = 1; b = 0; c = 1;
        #20; a = 1; b = 1; c = 0;
        #20; a = 1; b = 1; c = 1;
    end

endmodule // MajorityTest
```

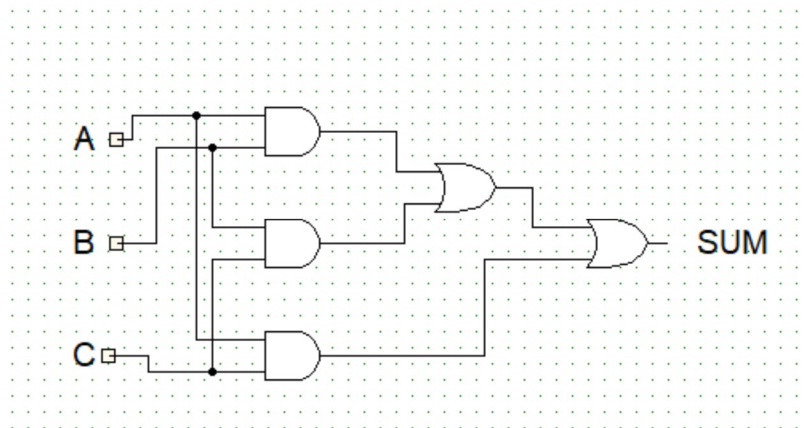

```
iverilog.exe src/majority.v && vvp.exe a.out
a = 0, b = 0, c = 0, sum = 0
a = 0, b = 0, c = 1, sum = 0
a = 0, b = 1, c = 0, sum = 0
a = 0, b = 1, c = 1, sum = 1
a = 1, b = 0, c = 0, sum = 0
```

```

a = 1, b = 0, c = 1, sum = 1
a = 1, b = 1, c = 0, sum = 1
a = 1, b = 1, c = 1, sum = 1

```

---

## Problem 2

A conditional inverter is an XOR gate with exactly two unique inputs. It, like all functions, can be broken down into ANDs, ORs, and NOTs.

<i>a</i>	<i>b</i>	<i>out</i>
0	0	<b>0</b>
0	1	<b>1</b>
1	0	<b>1</b>
1	1	<b>0</b>

		<i>b</i>	
		0	1
	0	0	1
<i>a</i>	1	1	0

---

```

module Inverter(
    input wire lhs,
    input wire rhs,
    output wire out
);

    // Invert left and right hand sides
    not(lhs_prime, lhs);
    not(rhs_prime, rhs);

    // Compute products
    and(left, lhs_prime, rhs);
    and(right, lhs, rhs_prime);

    // Compute sum
    or(out, left, right);

```

```
endmodule // Inverter


module InverterTest;

    reg lhs;
    reg rhs;
    wire out;

    Inverter inverter(lhs, rhs, out);

    initial begin
        $monitor("lhs = %d, rhs = %d, out = %d", lhs, rhs, out);
        lhs = 0; rhs = 0;
        #20; lhs = 0; rhs = 1;
        #20; lhs = 1; rhs = 0;
        #20; lhs = 1; rhs = 1;
    end

endmodule // InverterTest
```

 

```
iverilog.exe src/inverter.v && vvp.exe a.out
lhs = 0, rhs = 0, out = 0
lhs = 0, rhs = 1, out = 1
lhs = 1, rhs = 0, out = 1
lhs = 1, rhs = 1, out = 0
```

### Problem 3

A simple two input multiplexer is a  $2 \times 1$  multiplexer where  $a$  and  $b$  are inputs and  $c$  is the control. This function can be implemented easily using only AND, OR, and NOT gates.

<i>a</i>	<i>b</i>	<i>c</i>	<i>out</i> )
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

	<i>bc</i>			
	00	01	11	10
<i>a</i> 0	0	0	1	0
1	1	0	1	1

```

module Multiplexer(
    input wire a,
    input wire b,
    input wire c,
    output wire out
);

    // Invert control input
    not(c_prime, c);

    // Compute products
    and(left, a, c_prime);
    and(right, b, c);

    // Compute sum
    or(out, left, right);


endmodule // Multiplexer
    
```

```

module MultiplexerTest;

    reg a;
    
```

```
reg b;  
reg c;  
wire out;  
  
Multiplexer multiplexer(a, b, c, out);  
  
initial begin  
    $monitor("a = %d, b = %d, c = %d, out = %d", a, b, c, out);  
    a = 0; b = 0; c = 0;  
    #20; a = 0; b = 0; c = 1;  
    #20; a = 0; b = 1; c = 0;  
    #20; a = 0; b = 1; c = 1;  
    #20; a = 1; b = 0; c = 0;  
    #20; a = 1; b = 0; c = 1;  
    #20; a = 1; b = 1; c = 0;  
    #20; a = 1; b = 1; c = 1;  
end  
  
endmodule // MultiplexerTest
```

 

```
iverilog.exe src/multiplexer.v && vvp.exe a.out  
a = 0, b = 0, c = 0, out = 0  
a = 0, b = 0, c = 1, out = 0  
a = 0, b = 1, c = 0, out = 0  
a = 0, b = 1, c = 1, out = 1  
a = 1, b = 0, c = 0, out = 1  
a = 1, b = 0, c = 1, out = 0  
a = 1, b = 1, c = 0, out = 1  
a = 1, b = 1, c = 1, out = 1
```

## Problem 4

The one bit half adder is a circuit with two inputs and two outputs. It computes both the sum and the carry given both the left and right hand sides as binary inputs. The construction of this circuit can be greatly simplified through the use of an XOR gate.

Sum (conditional inverter)

$a$	$b$	$sum$
0	0	<b>0</b>
0	1	<b>1</b>
1	0	<b>1</b>
1	1	<b>0</b>

		$b$	
		0	1
$a$	0	0	1
	1	1	0

Carry (AND)

$a$	$b$	$Carry$
0	0	<b>0</b>
0	1	<b>0</b>
1	0	<b>0</b>
1	1	<b>1</b>

		$b$	
		0	1
$a$	0	0	0
	1	0	1

---

```
module OneBitHalfAdder(
    input wire lhs,
    input wire rhs,
    output wire sum,
    output wire carry
);

    // Compute the sum
    xor(sum, lhs, rhs);

    // Compute the carry
    and(carry, lhs, rhs);

endmodule // OneBitHalfAdder

module OneBitHalfAdderTest;

    reg lhs;
    reg rhs;
    wire sum;
    wire carry;


    OneBitHalfAdder oneBitHalfAdder(lhs, rhs, sum, carry);

    initial begin
        $monitor("lhs = %d, rhs = %d, sum = %d, carry = %d", lhs,
            rhs, sum, carry);
        lhs = 0; rhs = 0;
        #20; lhs = 0; rhs = 1;
        #20; lhs = 1; rhs = 0;
        #20; lhs = 1; rhs = 1;
    end

endmodule // OneBitHalfAdderTest
```

---



 

---

```
iverilog.exe src/one_bit_half_adder.v && vvp.exe a.out
lhs = 0, rhs = 0, sum = 0, carry = 0
lhs = 0, rhs = 1, sum = 1, carry = 0
lhs = 1, rhs = 0, sum = 1, carry = 0
lhs = 1, rhs = 1, sum = 0, carry = 1
```

---

## Problem 5

By cascading the sums of two half-adder modules and ORing the carries of both modules, a full adder can be constructed out of two simple half adders.

---

```
module OneBitHalfAdder(
    input wire lhs,
    input wire rhs,
    output wire sum,
    output wire carry
);

    // Compute the sum
    xor(sum, lhs, rhs);

    // Compute the carry
    and(carry, lhs, rhs);

endmodule // OneBitHalfAdder

module OneBitFullAdder(
    input wire cin,
    input wire lhs,
```

```
    input wire rhs,
    output wire sum,
    output wire cout
);

    // Initilize two half-adders
    OneBitHalfAdder halfAdderA(lhs, rhs, buffer, carry_left);
    OneBitHalfAdder halfAdderB(buffer, cin, sum, carry_right);

    // Compute the carry
    or(cout, carry_left, carry_right);

endmodule // OneBitFullAdder

module OneBitFullAdderTest;


    reg cin;
    reg lhs;
    reg rhs;
    wire sum;
    wire cout;

    OneBitFullAdder oneBitFullAdder(cin, lhs, rhs, sum, cout);

    initial begin
        $monitor("cin = %d, lhs = %d, rhs = %d, sum = %d, cout = %d",
            cin, lhs, rhs, sum, cout);
        cin = 0; lhs = 0; rhs = 0;
        #20; cin = 0; lhs = 0; rhs = 1;
        #20; cin = 0; lhs = 1; rhs = 0;
        #20; cin = 0; lhs = 1; rhs = 1;
        #20; cin = 1; lhs = 0; rhs = 0;
        #20; cin = 1; lhs = 0; rhs = 1;
        #20; cin = 1; lhs = 1; rhs = 0;
        #20; cin = 1; lhs = 1; rhs = 1;
    end

endmodule // OneBitFullAdderTest
```

---

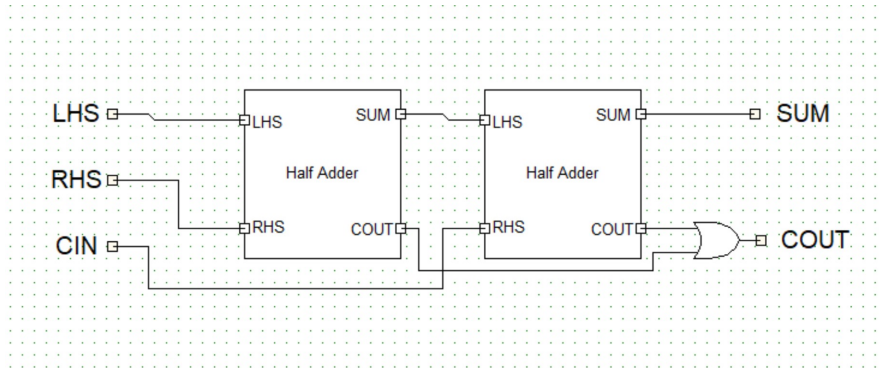


---

```

iverilog.exe src/one_bit_full_adder.v && vvp.exe a.out
cin = 0, lhs = 0, rhs = 0, sum = 0, cout = 0
cin = 0, lhs = 0, rhs = 1, sum = 1, cout = 0
cin = 0, lhs = 1, rhs = 0, sum = 1, cout = 0
cin = 0, lhs = 1, rhs = 1, sum = 0, cout = 1
cin = 1, lhs = 0, rhs = 0, sum = 1, cout = 0
cin = 1, lhs = 0, rhs = 1, sum = 0, cout = 1
cin = 1, lhs = 1, rhs = 0, sum = 0, cout = 1
cin = 1, lhs = 1, rhs = 1, sum = 1, cout = 1
  
```

---

## Problem 6

A full adder can be implemented directly (without chaining half-adders). The full adder takes three inputs (left-hand-side, right-hand-side, and carry-in). and produces sum and carry-out values.

<i>x</i>	<i>y</i>	<i>z</i>	<i>sum</i>	<i>cout</i>
0	0	0	<b>0</b>	<b>0</b>
0	0	1	<b>1</b>	<b>0</b>
0	1	0	<b>1</b>	<b>0</b>
0	1	1	<b>0</b>	<b>1</b>
1	0	0	<b>1</b>	<b>0</b>
1	0	1	<b>0</b>	<b>1</b>
1	1	0	<b>0</b>	<b>1</b>
1	1	1	<b>1</b>	<b>1</b>

		<i>yz</i>			
		00	01	11	10
<i>x</i>	0	0	1	0	1
	1	1	0	1	0

		<i>yz</i>			
		00	01	11	10
<i>x</i>	0	0	0	1	0
	1	0	1	1	1

---

```

module OneBitFullAdderDirect(
    input wire lhs,
    input wire rhs,
    input wire cin,
    output wire sum,
    output wire cout
);

    // Invert inputs
    not(lhs_, lhs);
    not(rhs_, rhs);
    not(cin_, cin);

    // Compute sum products
    and(lhs_rhs_, lhs_, rhs_);
    and(lhs_cin_, lhs_, cin_);
    and(rhs_cin_, rhs_, cin_);
    and(rhslhs, rhs, lhs);

    and(lhs_rhs_cin, lhs_rhs_, cin);
    and(lhs_cin_rhs, lhs_cin_, rhs);
    and(rhs_cin_lhs, rhs_cin_, lhs);
    and(rhslhscin, rhslhs, cin);

```

```
// Compute cout products
and(rhs_and_cin, rhs, cin);
and(lhs_and_cin, lhs, cin);
and(lhs_and_rhs, lhs, rhs);

// Compute sum sums
or(left_sum_buffer, lhs_rhs_cin, lhs_cin_rhs);
or(right_sum_buffer, rhs_cin_lhs, rhslhs_cin);
or(sum, left_sum_buffer, right_sum_buffer);

// Compute cout sums
or(cout_buffer, rhs_and_cin, lhs_and_cin);
or(cout, cout_buffer, lhs_and_rhs);

endmodule // OneBitFullAdderDirect

module OneBitFullAdderDirectTest;


  reg cin;
  reg lhs;
  reg rhs;
  wire sum;
  wire cout;

  OneBitFullAdderDirect oneBitFullAdderDirect(lhs, rhs, cin,
    sum, cout);

  initial begin
    $monitor("cin = %d, lhs = %d, rhs = %d, sum = %d, cout = %d",
      cin, lhs, rhs, sum, cout);
    cin = 0; lhs = 0; rhs = 0;
    #20; cin = 0; lhs = 0; rhs = 1;
    #20; cin = 0; lhs = 1; rhs = 0;
    #20; cin = 0; lhs = 1; rhs = 1;
    #20; cin = 1; lhs = 0; rhs = 0;
    #20; cin = 1; lhs = 0; rhs = 1;
    #20; cin = 1; lhs = 1; rhs = 0;
    #20; cin = 1; lhs = 1; rhs = 1;
  end

endmodule // OneBitFullAdderDirectTest
```

---

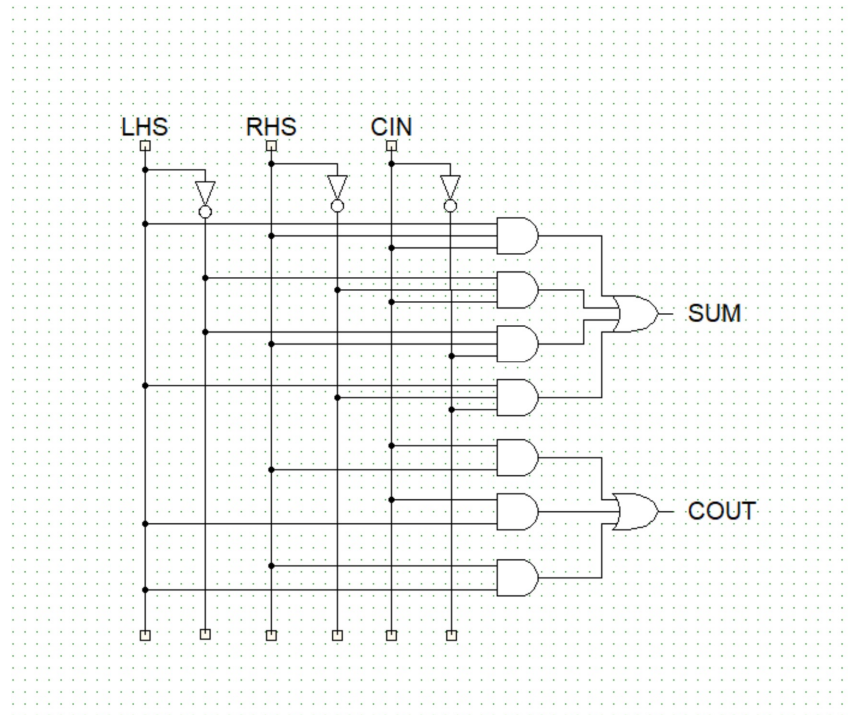


---

```

iverilog.exe src/one_bit_full_adder_direct.v && vvp.exe
a.out
cin = 0, lhs = 0, rhs = 0, sum = 0, cout = 0
cin = 0, lhs = 0, rhs = 1, sum = 1, cout = 0
cin = 0, lhs = 1, rhs = 0, sum = 1, cout = 0
cin = 0, lhs = 1, rhs = 1, sum = 0, cout = 1
cin = 1, lhs = 0, rhs = 0, sum = 1, cout = 0
cin = 1, lhs = 0, rhs = 1, sum = 0, cout = 1
cin = 1, lhs = 1, rhs = 0, sum = 0, cout = 1
cin = 1, lhs = 1, rhs = 1, sum = 1, cout = 1
  
```

---

## Problem 7

By using a control bit and XORing the right hand side, a cascaded adder can be used as a subtractor (by adding the 2's complement inverse). By cascading four one-bit full adders, a four-bit adder/subtractor can be created. If the c2 and cout lines have different values, then an overflow must have occurred.

---

```

module OneBitFullAdderDirect(
  
```

```
    input wire lhs,
    input wire rhs,
    input wire cin,
    output wire sum,
    output wire cout
);

// Invert inputs
not(lhs_, lhs);
not(rhs_, rhs);
not(cin_, cin);

// Compute sum products
and(lhs_rhs_, lhs_, rhs_);
and(lhs_cin_, lhs_, cin_);
and(rhs_cin_, rhs_, cin_);
and(rhslhs, rhs, lhs);

and(lhs_rhs_cin, lhs_rhs_, cin);
and(lhs_cin_rhs, lhs_cin_, rhs);
and(rhs_cin_lhs, rhs_cin_, lhs);
and(rhslhscin, rhslhs, cin);

// Compute cout products
and(rhs_and_cin, rhs, cin);
and(lhs_and_cin, lhs, cin);
and(lhs_and_rhs, lhs, rhs);

// Compute sum sums
or(left_sum_buffer, lhs_rhs_cin, lhs_cin_rhs);
or(right_sum_buffer, rhs_cin_lhs, rhslhscin);
or(sum, left_sum_buffer, right_sum_buffer);

// Compute cout sums
or(cout_buffer, rhs_and_cin, lhs_and_cin);
or(cout, cout_buffer, lhs_and_rhs);

endmodule // OneBitFullAdderDirect

module FourBitAdder(
    input wire operation,
    input wire [3:0] lhs,
    input wire [3:0] rhs,
    output wire [3:0] sum,
    output wire cout,
```

```
    output wire overflow
);

// Carry wires
wire c0;
wire c1;
wire c2;

// XOR the right hand side with the operation
xor(rhs_0, rhs[0], operation);
xor(rhs_1, rhs[1], operation);
xor(rhs_2, rhs[2], operation);
xor(rhs_3, rhs[3], operation);

// Full adder modules
OneBitFullAdderDirect adder_0(lhs[0], rhs_0, operation,
    sum[0], c0);
OneBitFullAdderDirect adder_1(lhs[1], rhs_1, c0, sum[1], c1);
OneBitFullAdderDirect adder_2(lhs[2], rhs_2, c1, sum[2], c2);
OneBitFullAdderDirect adder_3(lhs[3], rhs_3, c2, sum[3], cout);

// Compute overflow
xor(overflow, cout, c2);

endmodule // FourBitAdder

module FourBitAdderTest;

    reg operation;
    reg signed [3:0] lhs;
    reg signed [3:0] rhs;
    wire signed [3:0] sum;
    wire cout;
    wire overflow;

    FourBitAdder fourBitAdder(operation, lhs, rhs, sum, cout,
        overflow);

    initial begin
        $monitor("op = %d, lhs = %d, rhs = %d, sum = %d, cout = %d,
            overflow = %d", operation, lhs, rhs, sum, cout, overflow);
        operation = 0; lhs = 5; rhs = 3;
        #20; operation = 0; lhs = 5; rhs = 0;
        #20; operation = 0; lhs = 5; rhs = -6;
        #20; operation = 1; lhs = 3; rhs = -3;
    end
endmodule
```




```

#20; operation = 1; lhs = 4; rhs = 2;
#20; operation = 0; lhs = 6; rhs = 7;
#20; operation = 0; lhs = 0; rhs = 0;
#20; operation = 1; lhs = 0; rhs = 0;
end

endmodule // FourBitAdderTest

```

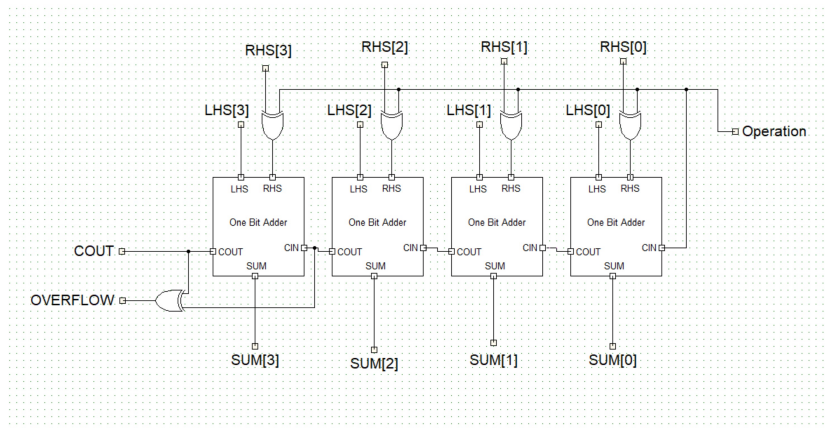

```

iverilog.exe src/four_bit_adder.v && vvp.exe a.out
op = 0, lhs = 5, rhs = 3, sum = -8, cout = 0, overflow = 1
op = 0, lhs = 5, rhs = 0, sum = 5, cout = 0, overflow = 0
op = 0, lhs = 5, rhs = -6, sum = -1, cout = 0, overflow =
0
op = 1, lhs = 3, rhs = -3, sum = 6, cout = 0, overflow = 0
op = 1, lhs = 4, rhs = 2, sum = 2, cout = 1, overflow = 0
op = 0, lhs = 6, rhs = 7, sum = -3, cout = 0, overflow = 1
op = 0, lhs = 0, rhs = 0, sum = 0, cout = 0, overflow = 0
op = 1, lhs = 0, rhs = 0, sum = 0, cout = 1, overflow = 0

```

## Problem Extra

The seven segment LED driver can be implemented as seven separate functions, one for each segment of the LED display (a..g).

$x$	$y$	$z$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	1	1	1	1	1	1	0
0	0	1	0	1	1	0	0	0	0
0	1	0	1	0	1	1	0	1	1
0	1	1	1	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	0	1	1	1	1	1	0	1	1
1	1	0	1	0	1	1	1	1	1
1	1	1	1	1	1	0	0	0	0

		$yz$			
		00	01	11	10
$x$	0	1	0	1	1
	1	0	1	1	1

		$yz$			
		00	01	11	10
$x$	0	1	1	0	0
	1	1	1	1	0

		$yz$			
		00	01	11	10
$x$	0	1	1	0	1
	1	1	1	1	1

		<i>yz</i>			
		00	01	11	10
<i>x</i>	0	1	0	1	1
	1	0	1	0	1

		<i>yz</i>			
		00	01	11	10
<i>x</i>	0	1	0	1	0
	1	0	0	0	1

		<i>yz</i>			
		00	01	11	10
<i>x</i>	0	1	0	1	1
	1	1	1	0	1

		<i>yz</i>			
		00	01	11	10
<i>x</i>	0	0	0	1	1
	1	1	1	0	1

---

```

module SevenSegment(
  input wire x,

```

```
input wire y,
input wire z,
output wire a,
output wire b,
output wire c,
output wire d,
output wire e,
output wire f,
output wire g
);

// Invert inputs
not(x_, x);
not(y_, y);
not(z_, z);

// Compute minimum products
and(x_Az_, x_, z_);
and(xAz, x, z);
and(x_Ay, x_, y);
and(xAy_Az, xAz, y_);
and(yAz_, y, z_);
and(x_Ay_Az_, x_Az_, y_);
and(x_AyAz, x_Ay, z);
and(xAyAz_, x, yAz_);
and(xAy_, x, y_);

// Compute a
or(a_buffer_0, x_Az_, xAz);
or(a, a_buffer_0, y);

// Compute b
or(b, y_, xAz);

// Compute c
or(c_buffer_0, y_, x);
or(c, c_buffer_0, z_);

// Compute d
or(d_buffer_0, x_Az_, xAy_Az);
or(d_buffer_1, d_buffer_0, x_Ay);
or(d, d_buffer_1, yAz_);

// Compute e
or(e_buffer_0, x_Ay_Az_, x_AyAz);
or(e, e_buffer_0, xAyAz_);
```

```
// Compute f
or(f_buffer_0, x_Ay, xAy_);
or(f, f_buffer_0, z_);

// Compute g
or(g_buffer_0, x_Ay, yAz_);
or(g, g_buffer_0, xAy_);

endmodule // SevenSegment

module SevenSegmentTest;


  reg x;
  reg y;
  reg z;
  wire a;
  wire b;
  wire c;
  wire d;
  wire e;
  wire f;
  wire g;

  SevenSegment sevenSegment(x, y, z, a, b, c, d, e, f, g);

  initial begin
    $monitor("x = %d, y = %d, z = %d, a = %d, b = %d, c = %d, d = %d, e = %d, f = %d, g = %d", x, y, z, a, b, c, d, e, f, g);
    x = 0; y = 0; z = 0;
    #20; x = 0; y = 0; z = 1;
    #20; x = 0; y = 1; z = 0;
    #20; x = 0; y = 1; z = 1;
    #20; x = 1; y = 0; z = 0;
    #20; x = 1; y = 0; z = 1;
    #20; x = 1; y = 1; z = 0;
    #20; x = 1; y = 1; z = 1;
  end

endmodule // SevenSegmentTest
```

---

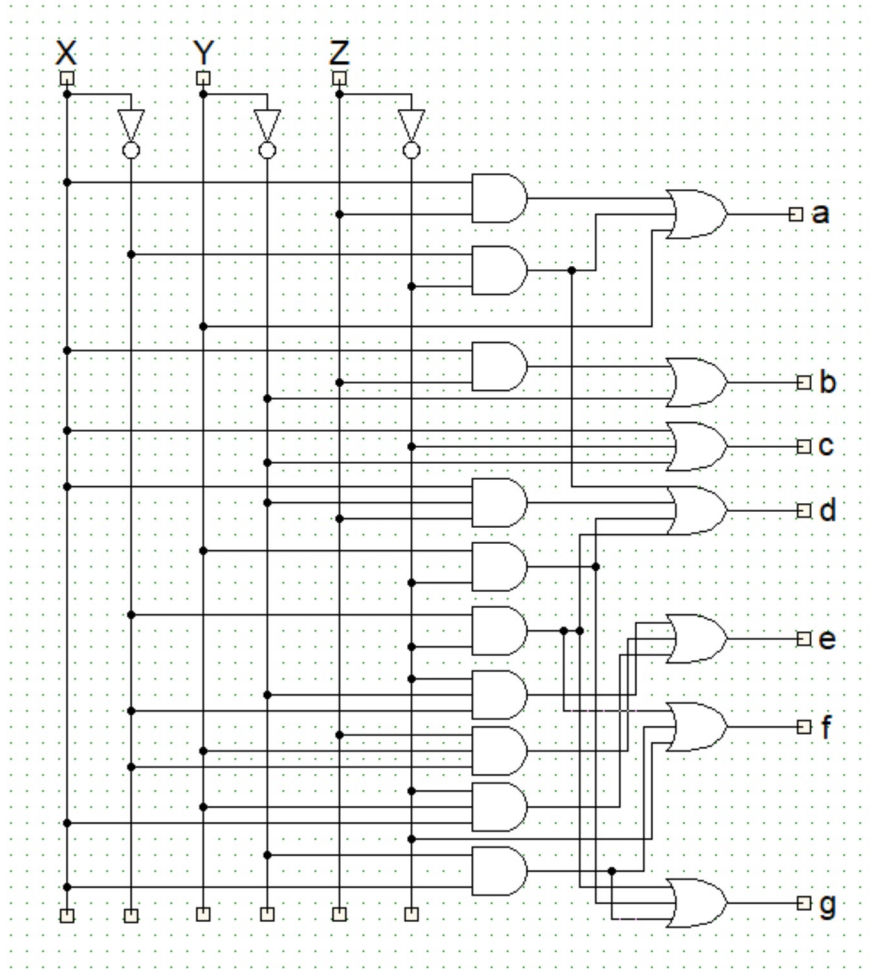

```

iverilog.exe src/seven_segment.v && vvp.exe a.out
x = 0, y = 0, z = 0, a = 1, b = 1, c = 1, d = 1, e = 1, f
= 1, g = 0
x = 0, y = 0, z = 1, a = 0, b = 1, c = 1, d = 0, e = 0, f
= 0, g = 0
x = 0, y = 1, z = 0, a = 1, b = 0, c = 1, d = 1, e = 0, f
= 1, g = 1
x = 0, y = 1, z = 1, a = 1, b = 0, c = 0, d = 1, e = 1, f
= 1, g = 1
x = 1, y = 0, z = 0, a = 0, b = 1, c = 1, d = 0, e = 0, f
= 1, g = 1
x = 1, y = 0, z = 1, a = 1, b = 1, c = 1, d = 1, e = 0, f
= 1, g = 1
x = 1, y = 1, z = 0, a = 1, b = 0, c = 1, d = 1, e = 1, f

```

$x = 1, y = 1, z = 1, a = 1, b = 1, c = 1, d = 0, e = 0, f = 0, g = 0$

---