

Problem 1

This simple CPU supports six operations: AND, OR, ADD, SUB, SLT, and LI. This CPU has four registers available to it: \$0, \$1, \$2, and \$3. Instructions are loaded into the instruction register. It should be noted that instructions can conform to two different formats, R-Type and L-Type, both of length nine. R-Type instructions follow the form: Opcode (3 bits), Lhs (2 bits), Rhs (2 bits), and destination (2 bits). L-Type instructions follow the form: Opcode (3 bits), Payload (4 bits), and destination (2 bits). An Li decoder is used in conjunction with several multiplexers to distinguish between L-Type and R-Type instructions. All of the actual operations are performed by the ALU, the rest of the CPU is simply moving and routing data around on the falling edge of each clock pulse. This data gets routed to the register file, which uses a register-select line to determine where the data on the write-data line should be routed.

```
module DLatch(  
    input wire enable,  
    input wire data,  
    output wire Q  
);  
  
    not(data_, data);  
    nand(x, data, enable);  
    nand(y, data_, enable);  
    nand(Q, x, Q1);  
    nand(Q1, y, Q);  
  
endmodule // DLatch  
  
module DFlipFlop(  
    input wire clk,  
    input wire data,  
    output wire Q  
);  
  
    not(clk_, clk);  
  
    DLatch d0(clk, data, y);  
    DLatch d1(clk_, y, Q);  
  
endmodule // DFlipFlop
```

```
module InstructionReg(  
    input wire clk,  
    input wire [8:0] dataIn,  
    output wire [8:0] dataOut  
);  
  
    DFlipFlop d0(clk, dataIn[0], dataOut[0]);  
    DFlipFlop d1(clk, dataIn[1], dataOut[1]);  
    DFlipFlop d2(clk, dataIn[2], dataOut[2]);  
    DFlipFlop d3(clk, dataIn[3], dataOut[3]);  
    DFlipFlop d4(clk, dataIn[4], dataOut[4]);  
    DFlipFlop d5(clk, dataIn[5], dataOut[5]);  
    DFlipFlop d6(clk, dataIn[6], dataOut[6]);  
    DFlipFlop d7(clk, dataIn[7], dataOut[7]);  
    DFlipFlop d8(clk, dataIn[8], dataOut[8]);
```

```
endmodule // InstructionReg
```

```
module HalfAdder(  
    input wire lhs,  
    input wire rhs,  
    output wire sum,  
    output wire cout  
);  
  
    // Compute sum  
    xor(sum, lhs, rhs);  
  
    // Comput cout  
    and(cout, lhs, rhs);
```

```
endmodule // HalfAdder
```

```
module Adder(  
    input wire cin,  
    input wire lhs,  
    input wire rhs,  
    output wire sum,  
    output wire cout  
);
```

```
// Instantiate two half-adders
HalfAdder halfAdderA(cin, lhs, buffer, carry_left);
HalfAdder halfAdderB(buffer, rhs, sum, carry_right);

// Compute cout
or(cout, carry_left, carry_right);

endmodule // Adder


module TwoOneMux(
    input wire select,
    input wire [1:0] data,
    output wire result
);

    // Invert select line
    not(select_, select);

    // Compute products
    and(lhs, data[0], select_);
    and(rhs, data[1], select);

    // Compute sum
    or(result, lhs, rhs);

endmodule // TwoOneMux


module FourOneMux(
    input wire [1:0] select,
    input wire [3:0] data,
    output wire result
);

    // Instantiate layer one
    TwoOneMux muxA(select[0], {data[0], data[1]}, AB);
    TwoOneMux muxB(select[0], {data[2], data[3]}, BC);

    // Instantiate layer two
    TwoOneMux muxC(select[1], {AB, BC}, result);

endmodule // FourOneMux
```

```
module OverflowDetector(  
    input wire lhs_msb,  
    input wire rhs_msb,  
    input wire sum_msb,  
    output wire overflow  
);  
  
    // Invert inputs  
    not(lhs_prime, lhs_msb);  
    not(rhs_prime, rhs_msb);  
    not(sum_prime, sum_msb);  
  
    // Condition one (positive operands, negative sum)  
    and(buffer_one, lhs_prime, rhs_prime);  
    and(condition_one, buffer_one, sum_msb);  
  
    // Condition two (negative operands, positive sum)  
    and(buffer_two, lhs_msb, rhs_msb);  
    and(condition_two, buffer_two, sum_prime);  
  
    // Compute overflow  
    or(overflow, condition_one, condition_two);  
  
endmodule // OverflowDetector  
  
module OneBitALU(  
    input wire rhs_invert,  
    input wire [1:0] opcode,  
    input wire cin,  
    input wire lhs,  
    input wire rhs,  
    input wire less,  
    output wire result,  
    output wire cout  
);  
  
    // Handle rhs inversion  
    not(rhs_, rhs);  
    TwoOneMux inverter(rhs_invert, {rhs_, rhs}, rhs_inverted);  
  
    // Instantiate output mux
```

```
FourOneMux mux(opcode, {and_out, or_out, sum_out, less},
    result);

// Instantiate operations
and(and_out, lhs, rhs_inverted);
or(or_out, lhs, rhs_inverted);
Adder adder(cin, lhs, rhs_inverted, sum_out, cout);

endmodule // OneBitALU

module OneBitALU_Set(
    input wire rhs_invert,
    input wire [1:0] opcode,
    input wire cin,
    input wire lhs,
    input wire rhs,
    input wire less,
    output wire result,
    output wire overflow,
    output wire set
);

// Handle rhs inversion
not(rhs_, rhs);
TwoOneMux inverter(rhs_invert, {rhs_, rhs}, rhs_inverted);

// Instantiate output mux
FourOneMux mux(opcode, {and_out, or_out, sum_out, less},
    result);

// Instantiate operations
and(and_out, lhs, rhs_inverted);
or(or_out, lhs, rhs_inverted);
Adder adder(cin, lhs, rhs_inverted, sum_out, cout); // NOTE:
    cout is unused in this block
buf(set, sum_out);

// Handle overflow detection
OverflowDetector detector(lhs, rhs_inverted, sum_out,
    overflow);

endmodule // OneBitALU_Set
```

```
module ALU(
    input wire [2:0] opcode,
    input wire [3:0] lhs,
    input wire [3:0] rhs,
    output wire [3:0] result,
    output wire overflow,
    output wire zero
);

    // Instantiate four one-bit ALUs
    OneBitALU aluA(opcode[2], {opcode[1], opcode[0]}, opcode[2],
        lhs[0], rhs[0], set, result[0], coutA);
    OneBitALU aluB(opcode[2], {opcode[1], opcode[0]}, coutA,
        lhs[1], rhs[1], 1'b0, result[1], coutB);
    OneBitALU aluC(opcode[2], {opcode[1], opcode[0]}, coutB,
        lhs[2], rhs[2], 1'b0, result[2], coutC);
    OneBitALU_Set aluD(opcode[2], {opcode[1], opcode[0]}, coutC,
        lhs[3], rhs[3], 1'b0, result[3], overflow_buffer, set);

    // Compute zero
    or(left, result[0], result[1]);
    or(right, result[2], result[3]);
    or(zero_, left, right);
    not(zero, zero_);

    // Limit overflow to arithmetic operations
    and(overflow, overflow_buffer, opcode[1]);

endmodule // ALU

module RegFile(
    input wire clk,
    input wire [1:0] readRegA,
    input wire [1:0] readRegB,
    input wire [1:0] writeReg,
    input wire [3:0] writeData,
    output wire [3:0] readDataA,
    output wire [3:0] readDataB
);

    reg [3:0] memory [0:3];

    assign readDataA = memory[readRegA];
```

```
    assign readDataB = memory[readRegB];

    initial memory[0] = 0;

    always @(negedge clk) begin
        memory[writeReg] <= writeData;
    end

endmodule // RegFile


module LiDecoder(
    input wire [2:0] opcode,
    output wire result
);

    // Invert lower two bits
    not(op0_, opcode[0]);
    not(op1_, opcode[1]);

    // Compute product
    and(lowerBits, op0_, op1_);
    and(result, lowerBits, opcode[2]);

endmodule // LiDecoder


module CPU(
    input wire clk,
    input wire [8:0] instruction,
    output wire [3:0] writeData
);

    wire [8:0] IR;
    wire [3:0] lhs;
    wire [3:0] rhs;
    wire [3:0] aluResult;

    // Instantiate instruction register
    InstructionReg instructionReg(clk, instruction, IR);

    // Instantiate register file
    RegFile regFile(clk, IR[5:4], IR[3:2], IR[1:0], writeData,
        lhs, rhs);
```

```

// Instantaite write-data mux
TwoOneMux twoOneMux0(liResult, {IR[2], aluResult[0]},
    writeData[0]);
TwoOneMux twoOneMux1(liResult, {IR[3], aluResult[1]},
    writeData[1]);
TwoOneMux twoOneMux2(liResult, {IR[4], aluResult[2]},
    writeData[2]);
TwoOneMux twoOneMux3(liResult, {IR[5], aluResult[3]},
    writeData[3]);

// Instatiate the ALU
ALU alu(IR[8:6], lhs, rhs, aluResult, overflow, zero);

// Instantiate the li-decoder
LiDecoder liDecoder(IR[8:6], liResult);

endmodule // CPU

module TestCPU;

    reg clk;
    reg [8:0] instruction;
    wire signed [3:0] writeData;

    CPU cpu(clk, instruction, writeData);

    initial begin
        $display("Instruction\tWriteData");
        $monitor("%b\t%b %d", instruction, writeData, writeData);
        #1; instruction = 9'b100111110; clk = 1; #1; clk = 0; //
            Load 15 -> $2
        #1; instruction = 9'b100100011; clk = 1; #1; clk = 0; //
            Load 8 -> $3
        #1; instruction = 9'b000101101; clk = 1; #1; clk = 0; //
            $2 & $3 -> $1
        #1; instruction = 9'b110011011; clk = 1; #1; clk = 0; //
            $1 - $2 -> $3
        #1; instruction = 9'b111110010; clk = 1; #1; clk = 0; //
            SLT $2, $3, $0
        #1; instruction = 9'b010101101; clk = 1; #1; clk = 0; //
            $2 + $3 -> $1
        #1; instruction = 9'b110000101; clk = 1; #1; clk = 0; //
            $0 - $1 -> $1
    end



```




```

    #1; instruction = 9'b001011011; clk = 1; #1; clk = 0;    //
        $1 | $2 -> $3
    end
endmodule // TestCPU

```

 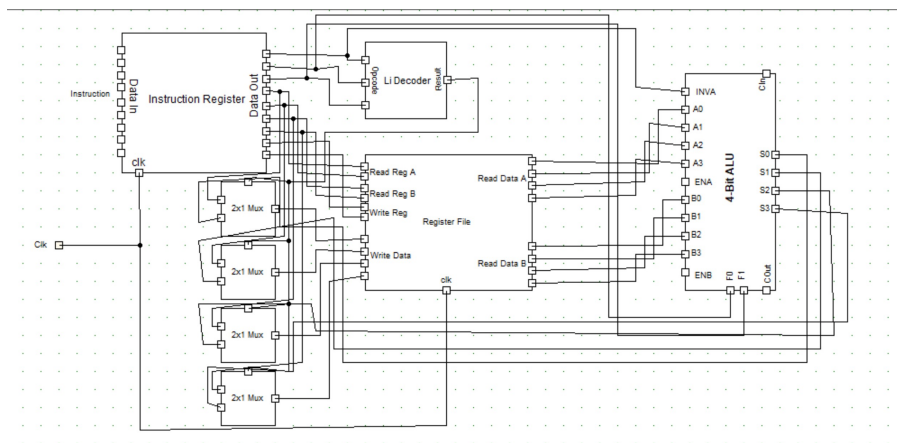

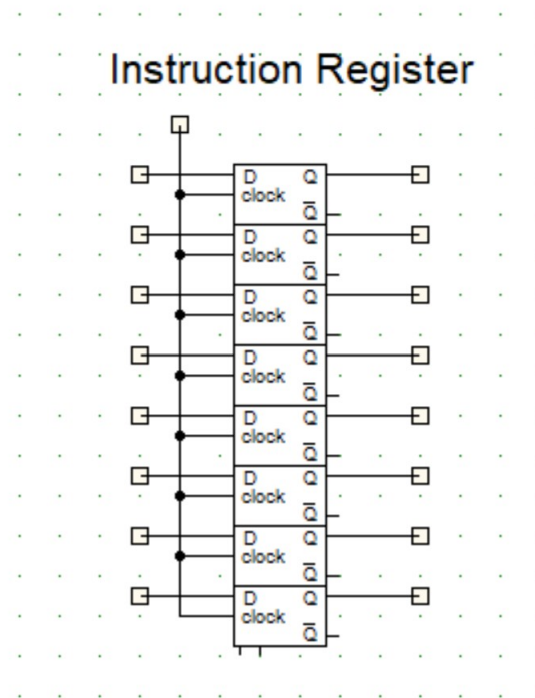

```

100111110    # Load 15 -> $2
100100011    # Load 8 -> $3
000101101    # $2 & $3 -> $1
110011011    # $1 - $2 -> $3
111110010    # SLT $2, $3, $0
010101101    # $2 + $3 -> $1
110000101    # $0 - $1 -> $1
001011011    # $1 | $2 -> $3
  
```

```

iverilog.exe ./CPU.v && vvp.exe a.out
Instruction  WriteData
xxxxxxxxx    xxxx  x
100111110    xxxx  x
100111110    1111 -1
100100011    1111 -1
100100011    1000 -8
000101101    1000 -8
000101101    1000 -8
110011011    1000 -8
  
```

Christopher Schmitt

110011011	1001 -7
111110010	1001 -7
111110010	0001 1
010101101	0001 1
010101101	1010 -6
110000101	1010 -6
110000101	0110 6
001011011	0110 6
001011011	0111 7
